
 


1 MUXes and Three-State Buffers (8pts)

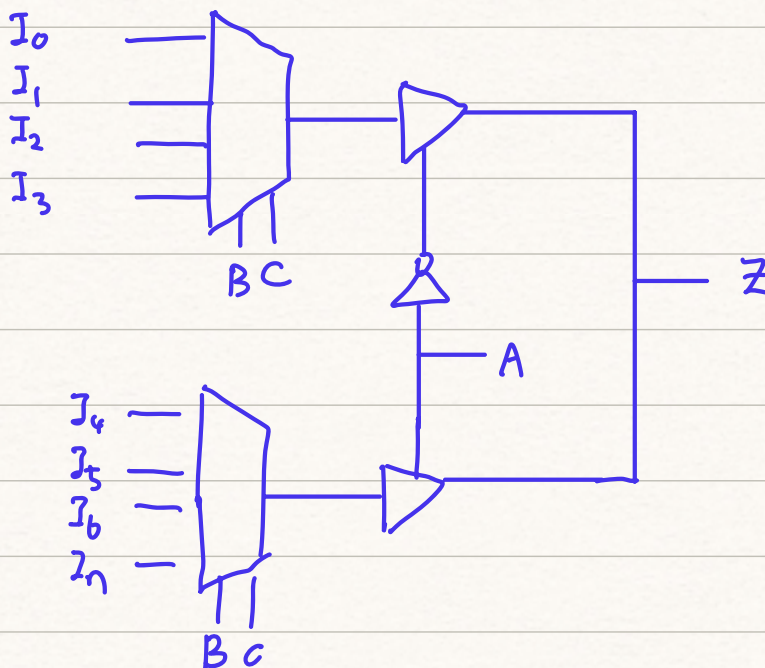Show how to make an 8-to-1 MUX using two 4-to-1 MUXes, two three-state buffers, and one inverter.




black box : use shannon expansion $Y = A(\dots) + A'(\dots)$



2 Latch I (8pts)

 Given the latch as below, complete the following truth table.




A	B	Q	Q^+
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

A	B	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

3 Latch II (16pts)

 A latch can be constructed from an OR gate, an AND gate, and an inverter connected as below.



1. What restriction must be placed on R and H so that P will always equal Q' (under steady-state conditions)?
2. Construct a next-state table and derive the minimum characteristic (next-state) equation for the latch.

1

1. check $P \neq Q'$ or $P = Q$

当 $Q = 1$ 且 $P = 1 \Rightarrow H = 0, R = 1$

当 $\underline{Q = 0}$ 且 $P = 0 \Rightarrow H = 1$ 且 $\underline{Q = 1}$ (矛盾, 不存在)

故 restriction: $(R, H) = (1, 0)$ #

2.

R	H	Q	Q^+
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	x
1	0	1	x
1	1	0	1
1	1	1	1

$H \backslash R$	0	1
0	0	x
0	0	x
1	1	1
1	0	1

because of 1.

$$Q^+ = R + HQ \#$$

4(1)

```

module cla_g1(
    output C3,          // carry output
    output[2:0] S,      // sum
    input[2:0] A, B,    // operands
    input C0            // carry input
);
// TODO:: Implement gate-level CLA

wire[2:0] P, G;

wire[3:0] C;

assign C[0] = C0;

assign C3 = C[3];

AND g0(G[0], A[0], B[0]);
AND g1(G[1], A[1], B[1]);
AND g2(G[2], A[2], B[2]);

OR g3(P[0], A[0], B[0]);
OR g4(P[1], A[1], B[1]);
OR g5(P[2], A[2], B[2]);


wire tmp1 , tmp2 , tmp3 ,tmp4 ,tmp5 ,tmp6 ;

//assign C[1] = G[0]+P[0]&C[0];
AND g6(tmp1,P[0],C[0]);
OR g7(C[1],G[0],tmp1);

//assign C[2] = G[1]+G[0]&P[1]+C[0]&P[0]&P[1];
AND4 g8(tmp2,C[0],P[0],P[1],1);
AND g9 (tmp3 , G[0],P[1]);
OR4 g10 (C[2],G[1],tmp2,tmp3,0);

//assign C[3] = G[2]+G[1]&P[2]+G[0]&P[1]&P[2]+C[0]&P[0]&P[1]&P[2];
AND4 g11(tmp4,C[0],P[0],P[1],P[2]);
AND4 g12 (tmp5,G[0],P[1],P[2],1);
AND g13(tmp6,G[1],P[2]);
OR4 g14(C[3],G[2],tmp6,tmp5,tmp4);


wire no_use[2:0];
FA b0(no_use[0], S[0], A[0], B[0], C[0]);
FA b1(no_use[1], S[1], A[1], B[1], C[1]);
FA b2(no_use[2], S[2], A[2], B[2], C[2]);

endmodule

```

4(2)

```

module rca_g1(
    output C3,          // carry output
    output[2:0] S,      // sum
    input[2:0] A, B,    // operands
    input C0            // carry input
);


// TODO:: Implement gate-level RCA
wire tmp[1:0];
FA a0(tmp[0], S[0], A[0], B[0], C0);
FA a1(tmp[1], S[1], A[1], B[1], tmp[0]);
FA a2(C3, S[2], A[2], B[2], tmp[1]);

endmodule

```

5 Lab 1: Waveform (12pts)

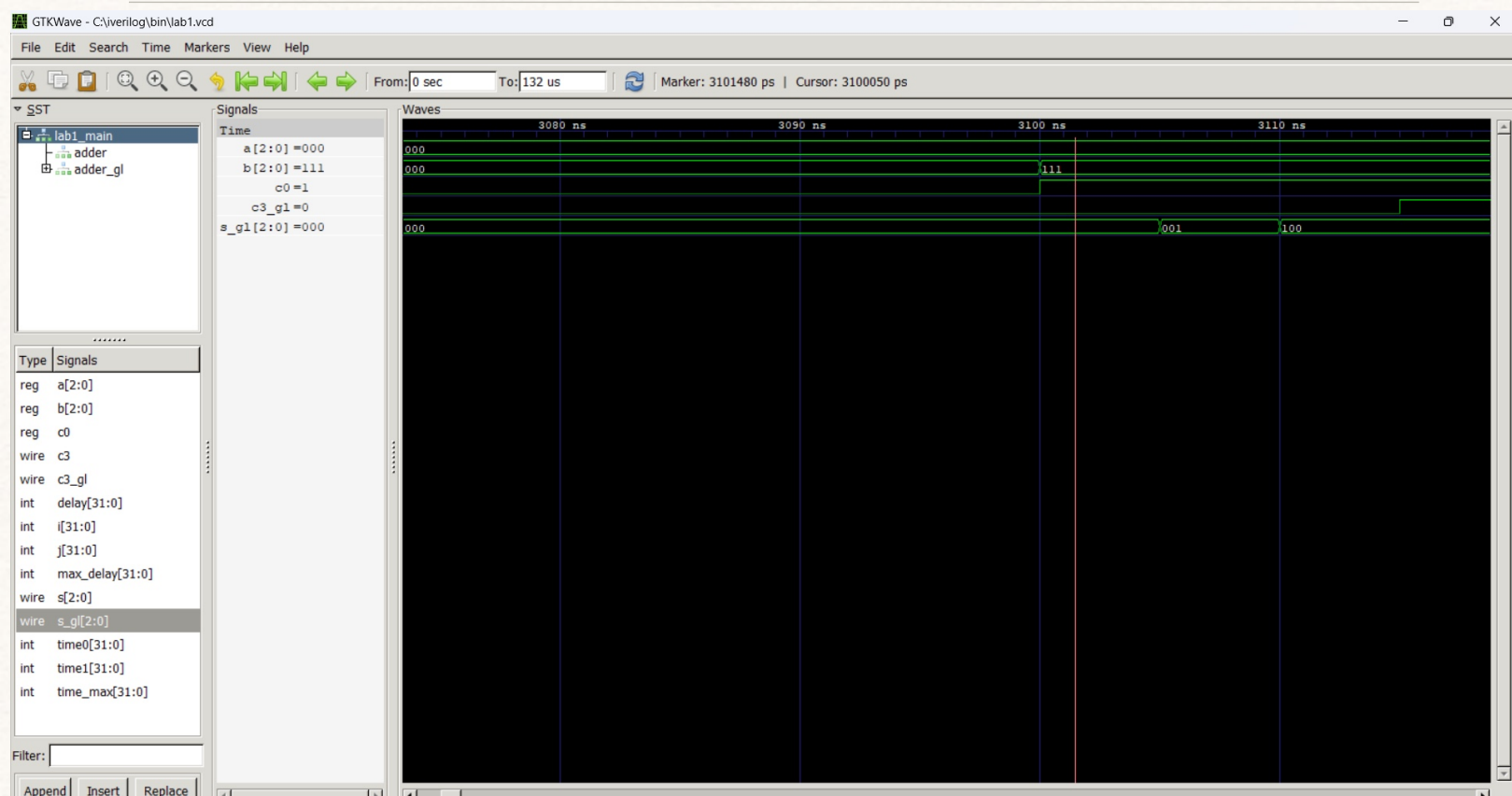Show the waveform of `cla_g1` on input transition from $000 + 000 + 0$ to $000 + 111 + 1$. You should select all the input and output signals of `cla_g1` module.



6 Lab 1: Propagation Delays (8pts)

1. (4pts) Find the maximum propagation delay of `rca_g1` and one of the corresponding input transitions.
2. (4pts) Find the maximum propagation delay of `cla_g1` and one of the corresponding input transitions.

1.

```
C:\iverilog\bin>vvp hw.vvp
VCD info: dumpfile lab1.vcd opened for output.
The maximum delay is 23 ticks on transition 000+000+0 --> 000+111+1
```

2.

```
C:\iverilog\bin>vvp hw.vvp
VCD info: dumpfile lab1.vcd opened for output.
The maximum delay is 20 ticks on transition 000+000+0 --> 000+011+1
```


7 Lab 1: Some Derivation (10pts)

Assume that only 2-input gates are used. Derive the number of levels needed in an n -bit carry-lookahead adder as a function of n .

已知 $g_i = A_i + B_i$ 都滿足 2-input : 1 level
 $p_i = A_i \oplus B_i$

$$\text{但 } C_{i+1} = g_i + p_i C_i$$

$$= g_i + p_i g_{i-1} + p_i p_{i-1} g_{i-2} + \dots \Rightarrow C_n \text{ 要 } n+1 \text{ 的加法}$$

$$\text{令 } G(i:j) = g_j + p_j g_{j-1} + p_j p_{j-1} g_{j-2} + \dots + (p_j \dots p_i g_i)$$

$$P(i:j) = (p_j \cdot p_{j-1} \cdot \dots \cdot p_i)$$

利用 binary tree 計算

$$\begin{cases} \square = P(k+1:j) \cdot G(i:k) : (\text{AND-gate}) \\ G(i:j) = G(k+1:j) + \square : (\text{OR-gate}) \end{cases}$$

需要 2 個 gate (level)

$$\text{故 } C_n = 2 \cdot \lceil \log_2(n+1) \rceil$$

2 個 gate = 2 level

$$\text{又 } S_i = A_i \oplus B_i \oplus \underbrace{C_i}_{\lceil \log_2 n \rceil} \Rightarrow 2 + \lceil \log_2 n \rceil \text{ 層}$$

故 total 層數 = max: $\left\{ 2 \lceil \log_2(n+1) \rceil + 1, 2 + 2 \lceil \log_2 n \rceil \right\}$ #1

$\underset{p.q}{\sim}$